



### Sheet (5) ..... Synchronous Machines


- 1) A 3- $\phi$ , Y-connected, wound rotor synchronous generator rated at 10 KVA, 230 V, 60 Hz has the following parameters,  $X_s = 2 \Omega$  / phase and  $R_s = 0.5 \Omega$  /per phase. The generator is connected to infinite bus. Calculate the percent voltage regulation at full load with 0.8 lagging power factor, 0.6 leading power factor and unity power factor.
- 2) A 230 V, 3- $\phi$ , Y-connected wound rotor synchronous generator gives on open circuit, e.m.f of 230 V, for afield current of 0.38 A. The same field current on short circuit causes an armature current of 12.5 A. The armature resistance measured between two lines is  $1.8 \Omega$ . Find the regulation for the current of 10 A at 0.8 lagging and 0.8 leading power factors.
- 3) A 230 V, 3- $\phi$ , Y-connected wound rotor synchronous motor has  $X_s = 3 \Omega$ / phase and  $R_s = 0.25 \Omega$ /phase. The motor operates on load such that the power angle is  $-15^\circ$ , and the excitation is so adjusted that the internally induced voltage is equal in magnitude to the terminal voltage. Determine:
- The armature current.
  - The power factor of the motor.

Best wishes  
Course committee:  
Dr. Abd Al-Wahab Hasan  
Eng. Mohamed Gamal  
Eng. Kotb Mohamed  
2013-2014

$$Z = R + jX$$



# Sheet 5

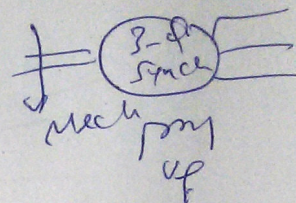

① Reg 1 V.R.


$10 \text{ KVA} = S$

$V_L = 230 \text{ V}$

$f = 60 \text{ Hz}$

$X_s = 2 \Omega$

$R_a = 0.5 \Omega$

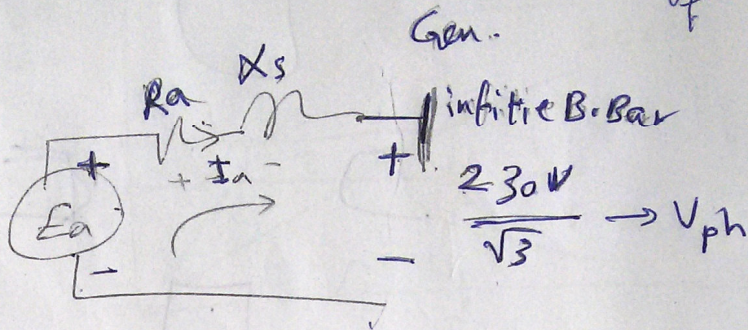

$$I_a = \frac{S}{\sqrt{3} V_L} = \frac{10 \times 10^3}{\sqrt{3} \times 230} = 25.102 \angle -30.27^\circ \text{ A}$$

$$V_{ph} = \frac{230}{\sqrt{3}} \angle 0^\circ = 132.79 \angle 0^\circ$$

$$\underset{\substack{\uparrow \\ E_{fL}}}{E_a} = \underset{\substack{\uparrow \\ E_{fL}}}{V_{ph}} + I_a (R_a + jX_s) = 176 \angle 10.68^\circ \text{ V}$$

$$\% \text{VR} = \frac{E_{aL} - V_{ph}}{V_{ph}} \times 100 = 32.53\% \quad \text{+ve} \rightarrow \text{for lag P.F.}$$

for lead P.F. = 0.6

$$\therefore I_a = 25.102 \angle \cos^{-1}(0.6) = 25.102 \angle 53.13^\circ \text{ A}$$

$$\therefore \underset{\substack{\uparrow \\ E_{fL}}}{E_a} = 107.91 \angle 21.85^\circ \text{ V}$$

$$\therefore \% \text{VR}_{\text{ge}} = \frac{107.91 - 132.79}{132.79} \times 100 = -18.73\% \rightarrow \text{-ve for lead P.F.}$$

for unity

$$I_a = 25.102 \angle 0^\circ$$

$$\therefore \underset{\substack{\uparrow \\ E_{fL}}}{E_a} = 135.142 \angle 10.7^\circ \text{ V}$$

$$\therefore \% \text{VR}_{\text{e}} = \frac{135.142 - 132.79}{132.79} \times 100 = 1.77\%$$



② Req VRY.

$$V_{ph} = \frac{230}{\sqrt{3}} = 132.79$$

$$I_f = 0.38 A$$

$$I_{sc} = 12.5 A$$

$$Z_s = \frac{230/\sqrt{3}}{12.5} = 10.6232$$

$$R_a = \frac{1.8}{2} = 0.9 \Omega$$

$$R_a = 0.9 \times 1.25 = 1.125 \Omega$$

$$X_s = \sqrt{Z_s^2 - R_a^2} = 10.5634 \Omega$$

$$I_a = 10 A$$

$$E_a = V_{ph} + I_a (R_a + jX_s) = 132.79 + j105.634$$

$$\text{at } 0.8 \text{ lag PF} : I_a = 10 / \cos^{-1}(0.8) = 12.5 A$$



$$E_{fL} = 219.411 \angle 20.7^\circ V$$

$$\%V_{Reg} = \frac{E_{fL} - E_{nL}}{E_{nL}} \times 100 = \frac{219.411 - 132.79}{132.79} \times 100 = 65.23\%$$

$$\text{at } 0.8 \text{ lead PF} : I_a = 10 / \cos^{-1}(0.8) = 12.5 A$$

$$E_{fL} = 120.316 \angle 49.3^\circ V$$
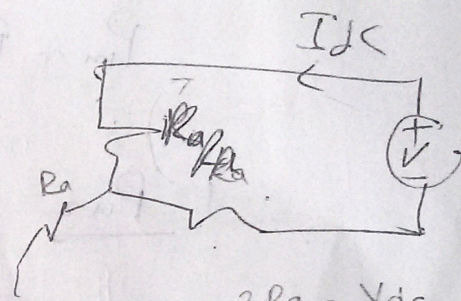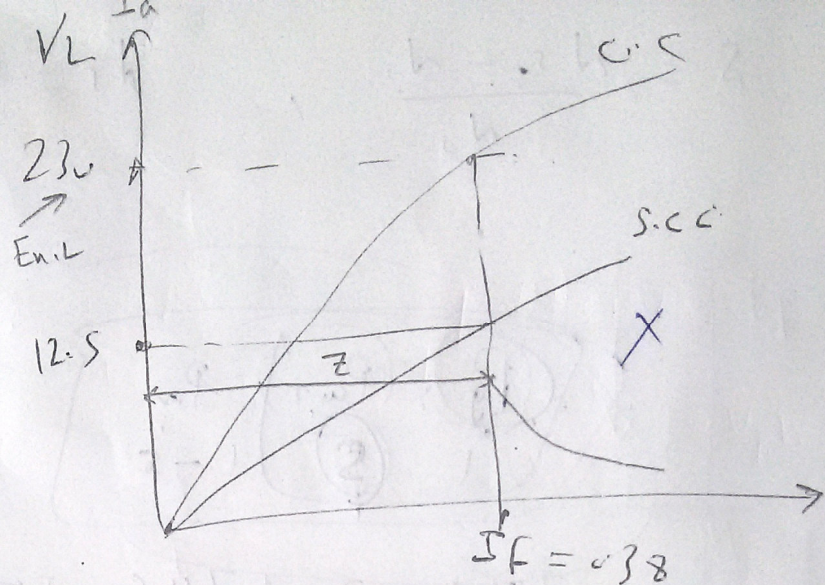
$$\%V_{Reg} = \frac{120.316 - 132.79}{132.79} \times 100 = -9.4\%$$



$$2R_a = \frac{V_{dc}}{I_{dc}} = 1.8$$

$$R_a = \frac{1.8}{2} = 0.9$$

$$R_{a,c} = 0.9 \times 1.25$$



③  $V_L = 230\text{ V}$

$X_s = 3\ \Omega$

$R_a = 0.25\ \Omega$

$\delta = -15^\circ$

$|E_a| = |V_{ph}|$


$V_{ph} = \frac{230}{\sqrt{3}} = \angle 0^\circ$

$E_a = \frac{230}{\sqrt{3}} \angle -15^\circ$

$E_a = V_{ph} - I_a (R_a + jX_s)$

$I_a = \frac{V_{ph} - E_a}{R_a + jX_s} = 11.515 \angle -2.736^\circ$

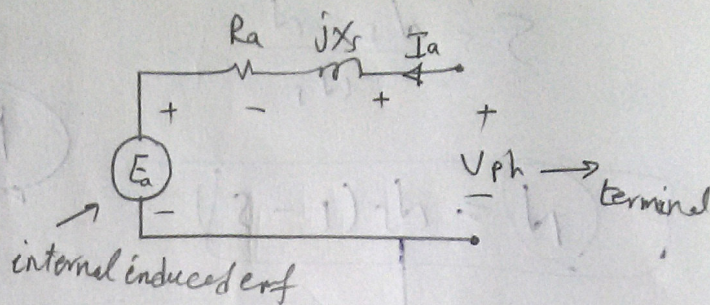p.f. =  $\cos(\angle V_{ph} - \angle I_a) = \cos(0 + 2.736)$   
 $= 0.9988 \text{ lag}$




$V_{ph} = V_t = I_a (R_a + jX_s) + E_a$

$\therefore I_a = \frac{V_t - E_a}{R_a + jX_s}$

$V_t = \frac{230}{\sqrt{3}} \angle 0^\circ \text{ V}$

$E_a = \frac{230}{\sqrt{3}} \angle -15^\circ \text{ V}$

$\therefore I_a =$

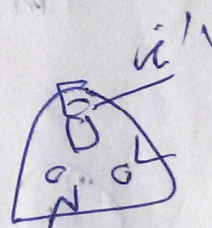



sheet (5)

① 8 pole 13-ph synch. Gen. Y-Conn.

168 slots with 9 cond./slot.  $N_r = 750 \text{ rpm}$ ,  $K_w = 0.96$

$E_{mof} = 1000 \text{ V}$  between lines.

Req:  $\phi = ?!$

Solution

$$E_{ph} = 4.44 * \phi * f * T_{ph} * K_w$$

where  $T_{ph} \rightarrow$  no. of turns per phase

$$Z = 168 * 9 = 1512 \text{ Conductors}$$

$$\text{no. of turns} = \frac{Z}{2} = 756 \text{ turns}$$

$$\therefore T_{ph} = \frac{756}{3} = 252 \text{ turns}$$

$$\therefore N_s = \frac{120 f}{P} \quad \therefore f = \frac{N_s * P}{120} = \frac{750 * 8}{120} = 50 \text{ Hz}$$

$\rightarrow = N_r$  for synch. machines

$$E_{ph} = \frac{1000}{\sqrt{3}} = 577.35 \text{ V}$$

$$\therefore \phi = \frac{E_{ph}}{4.44 * f * T_{ph} * K_w}$$

$$\therefore \phi = \frac{577.35}{4.44 * 50 * 252 * 0.96}$$

$$= 10.75 \text{ mWb}$$




②  $S_{\text{rated}} = 50 \text{ KVA}$ , Y-Conn.  $V_L = 440 \text{ V}$ ,  $f = 50 \text{ Hz}$ ,  $r_a = 0.25/\text{ph}$

$$X_a = 3.7 \Omega/\text{ph}$$

→ for unity P.f. & rated load:

- ①  $E_{\text{mf ph}}$     ②  $V_R\%$     ③ sketch phasor diagram

Solution

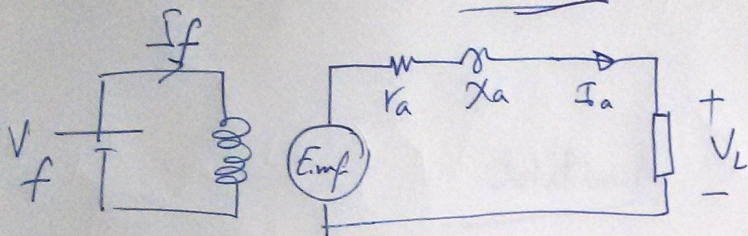

$$S = \sqrt{3} V_L I$$

$$= 3 V_{\text{ph}} I$$

$$E_{\text{mf ph}} = V_{\text{ph}} + I_a (r_a + jX_a)$$

assume the load voltage is the Ref.

$$\therefore V_{\text{ph}} = \frac{440}{\sqrt{3}} \angle 0^\circ = 254 \angle 0^\circ \text{ V}$$

$$I_a = \frac{S_{\text{rated}}}{\sqrt{3} \times 440} = 65.607 \angle 0^\circ \text{ A (unity P.f.)}$$

$$\therefore E_{\text{mf ph}} = 254 \angle 0^\circ + 65.607 \angle 0^\circ (0.25 + j3.7)$$


$$\therefore E_{\text{mf ph}} = 363.38 \angle 42^\circ \text{ V}$$

$42^\circ \rightarrow \delta$  load angle

$$\%V_R = \frac{E_{\text{mf fl}} - E_{\text{m n.l}}}{E_{\text{m n.l}}} \times 100 = \frac{363.38 - 254}{254} \times 100$$


$$\%V_R = 43\%$$

phasor diagram

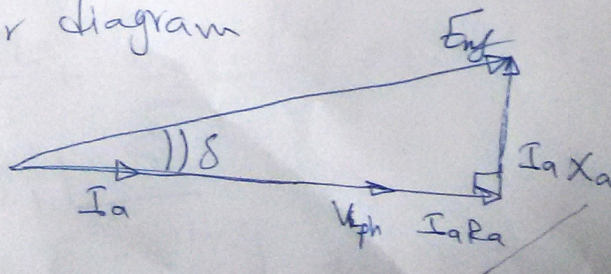



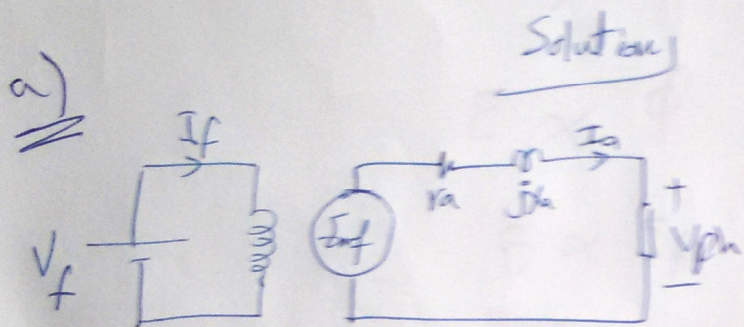③ 3ph gen.  $P_{rated} = 5 \text{ Kw} \rightarrow P_{out}$   $V_L = 110 \text{ V}, 29 \text{ A lag P.f.}$   
 $f = 50 \text{ Hz}, 1000 \text{ rpm}, r_a = 0.1 \Omega/\text{ph}, X_a = 1.53 \Omega/\text{ph}$   
 $- I_{f1}$  (Full load Current)  
Req ①  $E_{mf_{nl}}$ ,  $\%VR$ , Poles no.



Alternator  
 ssynch generator

at no-load

$$E_{mf_{nl}} = V_L / \sqrt{3} = \frac{110 \text{ V}}{\sqrt{3}}$$

$$N_s = \frac{120f}{P} = p = \frac{120f}{N_s} = \frac{120 \times 50}{1000} = 6 \text{ poles}$$

$$P = 3 V_{ph} I_{ph} \times \text{P.f.}$$

$$5 \times 10^3 = 3 \times \frac{110}{\sqrt{3}} \times 29 \times \text{P.f.}$$

$$\cos \phi = \text{P.f.} = \checkmark$$

$\phi = \checkmark$

$$E = V + I_a (r_a + jX_s)$$

$$= \frac{110}{\sqrt{3}} + 29 \angle -\phi \times (0.1 + j1.53)$$

$$E = \sqrt{\quad \quad \quad}$$

$$V_{reg\%} = \frac{E - 110/\sqrt{3}}{110/\sqrt{3}} \times 100 =$$

③



b)

$$I_{f2} = 0.9 I_{f1}$$

$$N_2 = N_1$$

$$E = 4.44 f \phi \underline{k_w} \underline{T_{p2}}$$

$$E \propto \underline{f} \phi$$

$$E \propto \phi$$

$$\phi \propto I_f$$

$$E_2 = 0.9 E_1 = \quad \checkmark$$

نفس

$$\underline{E_2} = V_2 + \underline{I_a} (r_a + jX_s)$$

نفس التيار دلتا زاوية

$$V_2 = \checkmark \quad || \quad \underline{\quad}$$

c)  $\underline{pf_3} = 0.8 \text{ lead}$

$$I = 25 \left( 1 + G_s^{-1} 0.8 \right)$$

نفس التيار (A) مع عاكس

نفس  $E_1$

$$E_3 = E_1$$